 


Digital Integrated Circuits & Microcontrollers


Chapter 3. Logic gates



1

Multiplexers (Data Selectors)

 
- A multiplexer has
 - N select inputs
 - 2^N data inputs
 - H output
- The selected data input is selected (routed) to the output.



2


Multiplexers

2-input multiplexer

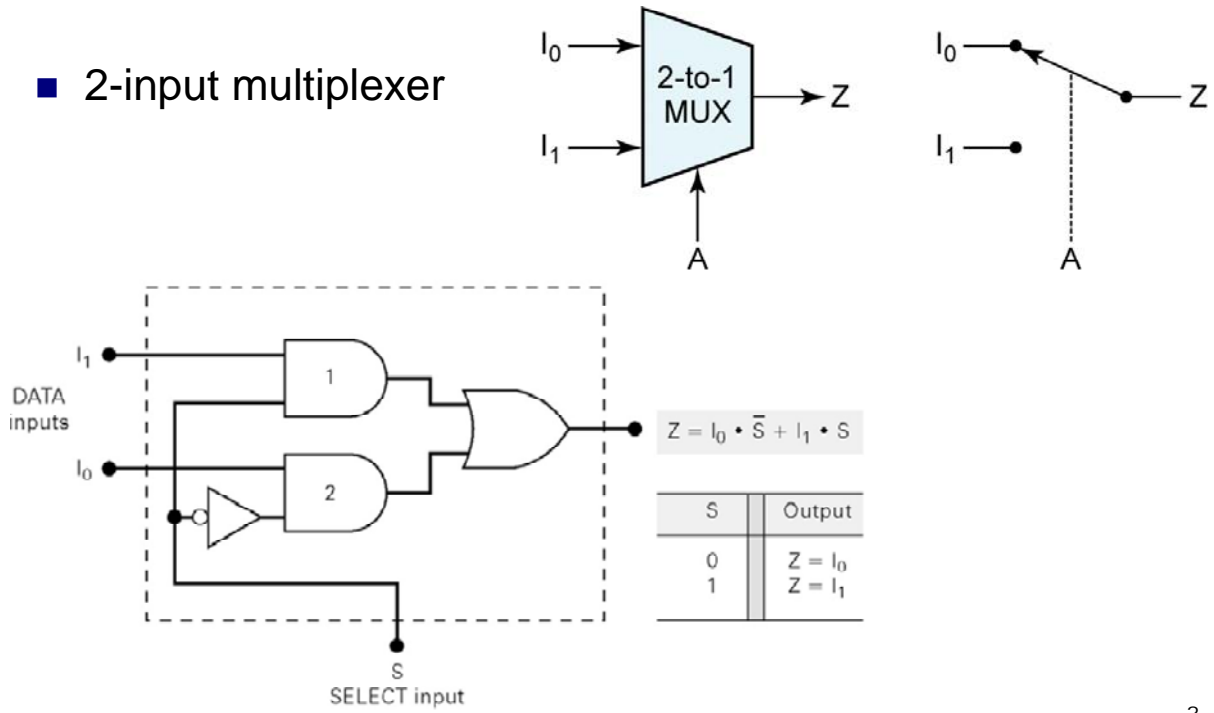


Multiplexers


4-input multiplexer

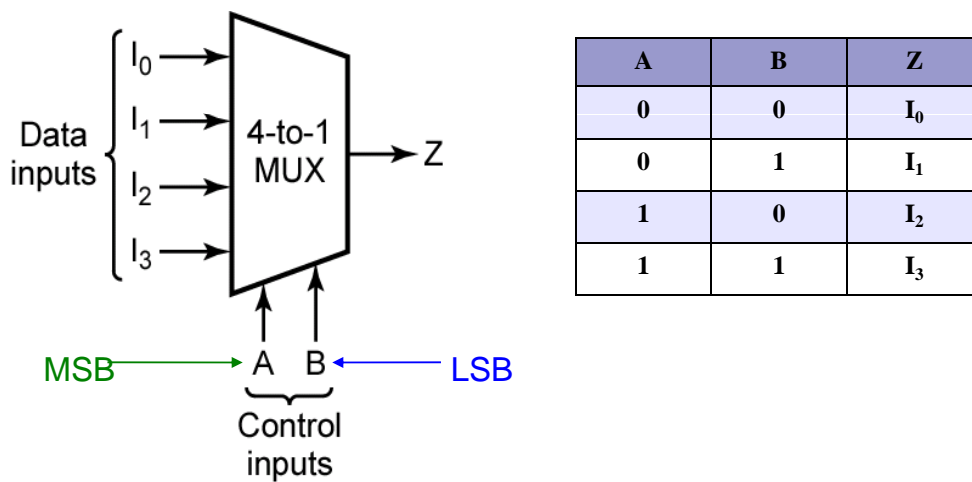

8 bit Multiplexer (74HC151)

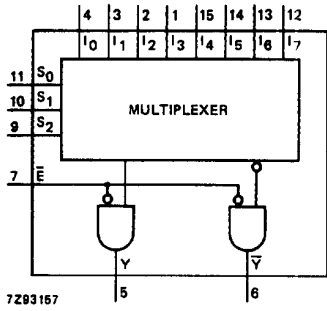


\bar{E}	S_2	S_1	S_0	Y
1	X	X	X	0
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7

 

Multiplexers

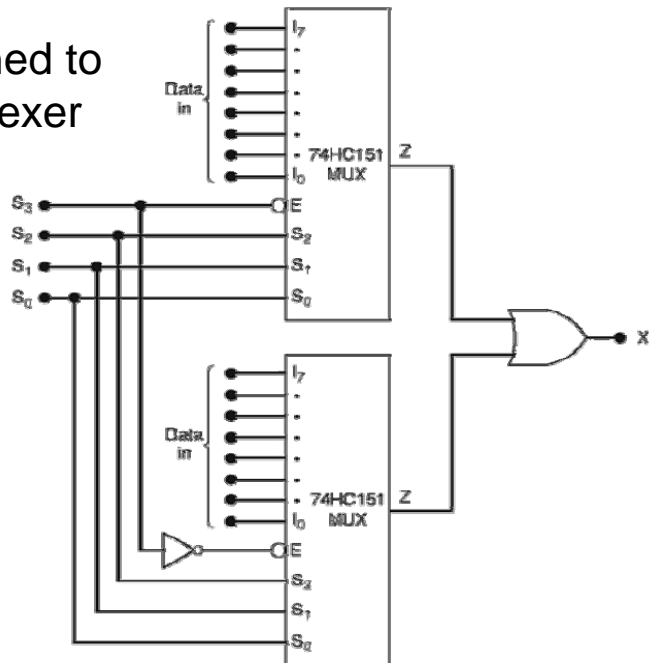
- two 74HC151s combined to form a 16-input multiplexer
- Exercise:
- Design a 16-to-1 multiplexer using 4-to-1 multiplexers only



Multiplexers used to Implement Logic Function

$$f = A\bar{B}\bar{C} + \bar{A}B\bar{C} + ABC$$


$$f = \sum (1, 2, 7)$$

 

7


Demultiplexers (Data Distributors)

 - A demultiplexer has
 - N control inputs
 - 1 data input
 - 2^N outputs
- A demultiplexer routes (or connects) the data input to the selected output.



8

Demultiplexers

 


A	B	W	X	Y	Z
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Decoders


- A decoder has
 - N inputs
 - 2^N outputs
- A decoder selects one of 2^N outputs by decoding the binary value on the N inputs.

Decoders

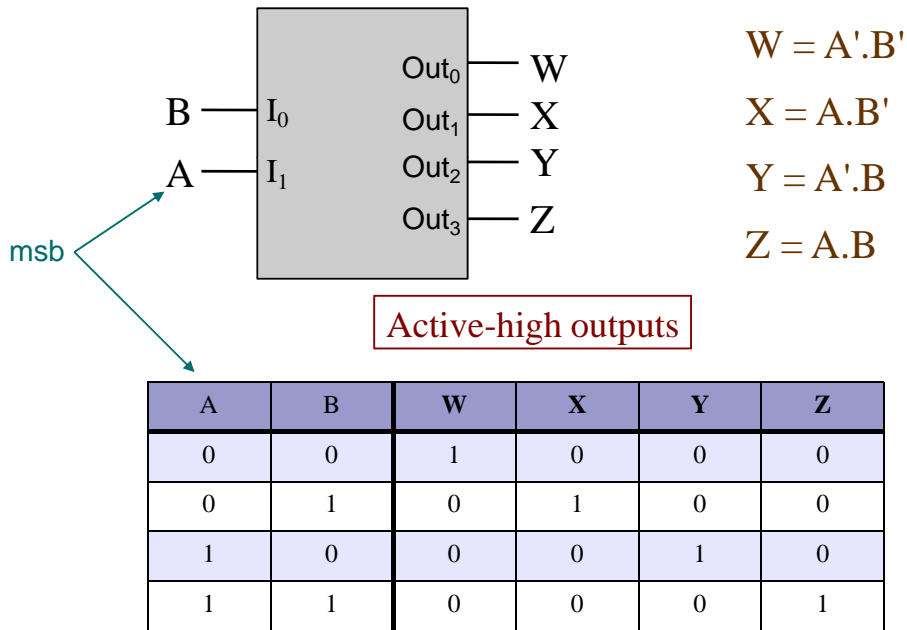

11

Decoders

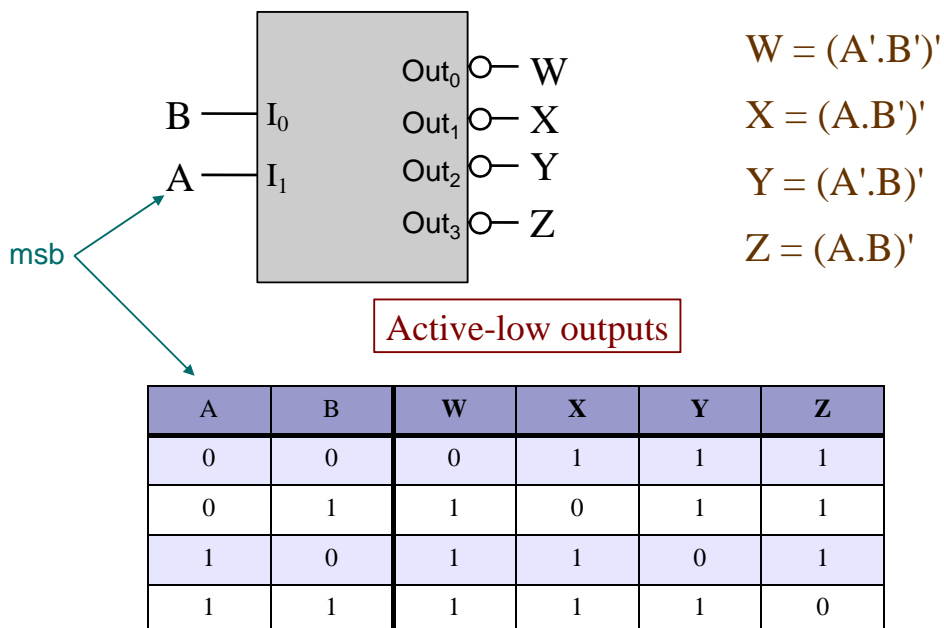



12

BCD (Binary Coded Decimal)

Decimal	Binary	HEX	BCD
0	0000	0	0000 0000
1	0001	1	0000 0001
2	0010	2	0000 0010
3	0011	3	0000 0011
4	0100	4	0000 0100
5	0101	5	0000 0101
6	0110	6	0000 0110
7	0111	7	0000 0111
8	1000	8	0000 1000
9	1001	9	0000 1001
10	01010	A	0001 0000
11	01011	B	0001 0001
12	01100	C	0001 0010
13	01101	D	0001 0011
14	01110	E	0001 0100
15	01111	F	0001 0101

BCD-to-7 Segment Display Decoder

Decimal digit	INPUTS DCBA	SEGMENT OUTPUTS
		a b c d e f g
0	0 0 0 0	1 1 1 1 1 1 0
1	0 0 0 1	0 1 1 0 0 0 0
2	0 0 1 0	1 1 0 1 1 0 1
3	0 0 1 1	1 1 1 1 0 0 1
4	0 1 0 0	0 1 1 0 0 1 1
5	0 1 0 1	1 0 1 1 0 1 1
6	0 1 1 0	1 0 1 1 1 1 1
7	0 1 1 1	1 1 1 0 0 0 0
8	1 0 0 0	1 1 1 1 1 1 1
9	1 0 0 1	1 1 1 1 0 1 1
10	1 0 1 0	X X X X X X X
11	1 0 1 1	X X X X X X X
12	1 1 0 0	X X X X X X X
13	1 1 0 1	X X X X X X X
14	1 1 1 0	X X X X X X X
15	1 1 1 1	X X X X X X X

  


Half Adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

 

15

Full Adder

A	B	C _i	S	C _o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + A.B.C_i$$

$$= A \oplus B \oplus C_i$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + ABC_i + ABC_i$$

$$= AB + AC_i + BC_i$$


$$= AB + C_i(A + B)$$

 

16


Full Adder from Half Adders

A	B	HA _S	HA _C	C _i	S	C _o
0	0	0	0	0	0	0
0	0	0	0	1	1	0
0	1	1	0	0	1	0
0	1	1	0	1	0	1
1	0	1	0	0	1	0
1	0	1	0	1	0	1
1	1	0	1	0	0	1
1	1	0	1	1	1	1

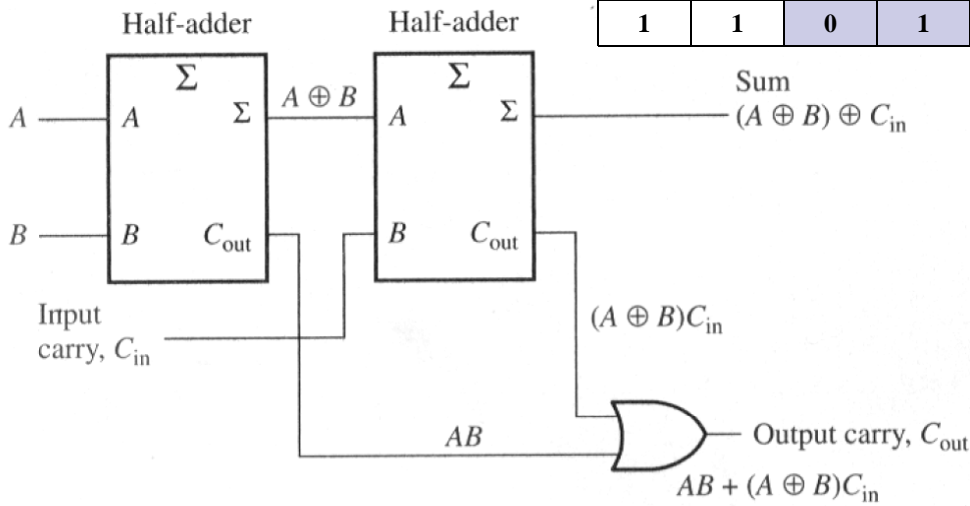

Parallel Adder

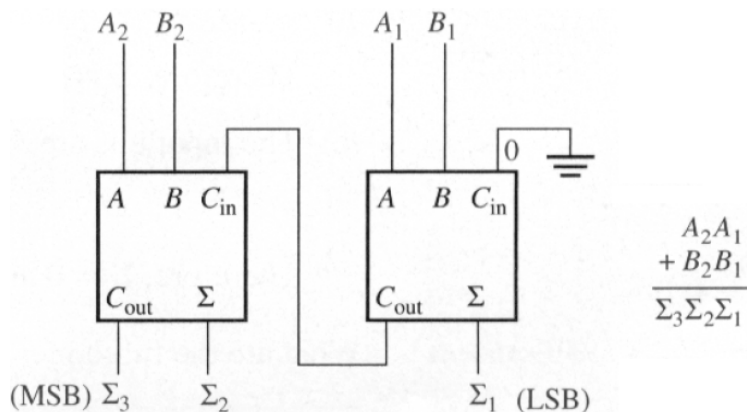- Uses 1 full adder per bit of the numbers
- The carry is propagated from one stage to the next most significant stage



4-bit Parallel Binary Adders

