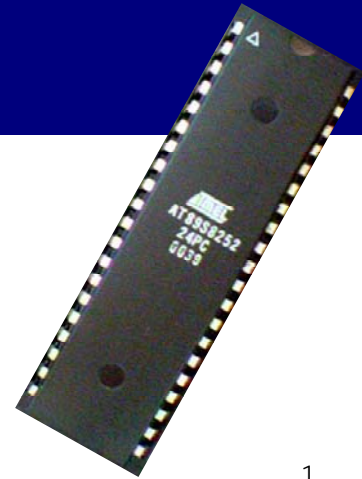


Digital Integrated Circuits & Microcontrollers

Chapter 4. Sequential Digital Circuits



1

Sequential Circuits

- **Combinational Logic**
 - the output(s) depends only on the current values of the input variables
- **Sequential Logic circuits**
 - the output(s) can depend on present and also past values of the input and the output variables
- **Sequential circuits exist in one of a defined number of states at any one time**
 - they move "sequentially" through a defined sequence of transitions from one state to the next

2



Synchronous and Asynchronous Sequential Logic

- Synchronous
 - the timing of all state transitions is controlled by a common clock
 - changes in all variables occur simultaneously
- Asynchronous
 - state transitions occur independently of any clock and normally dependent on the timing of transitions in the input variables
 - changes in more than one output do not necessarily occur simultaneously

3



Clock

- A clock signal is a square wave of fixed frequency
- Often, transitions will occur on one of the edges of clock pulses (i.e. the rising edge or the falling edge)


4

Flip-Flops

- Flip-flops (bistable) are the fundamental element of sequential circuits
- Flip-flops are essentially 1-bit storage devices
 - outputs can be set to store either 0 or 1 depending on the inputs
 - even when the inputs are de-asserted, the outputs retain their prescribed value
- Three main types of flip-flop:
 - SR, J-K, D

5


Flip-Flops

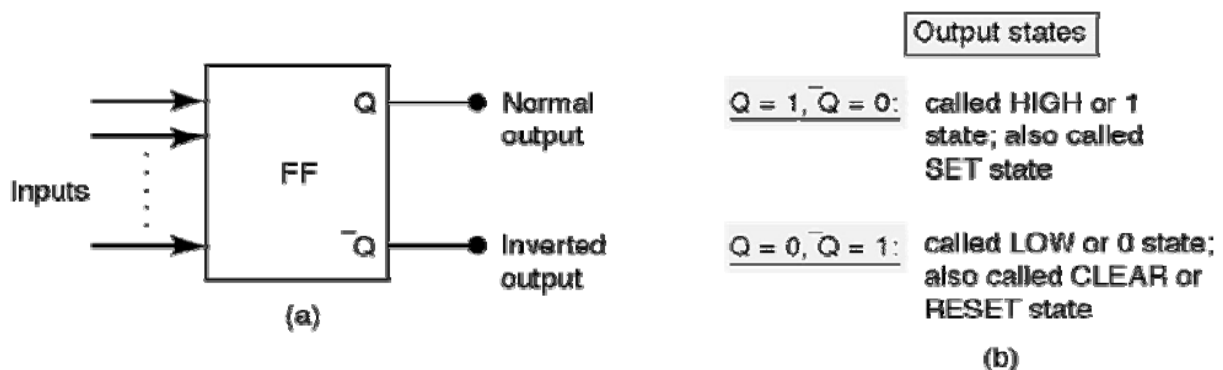

- Flip-flop (FF) = latch = bistable circuit

6


NAND SR Latch

 

- A NAND latch has two possible resting states when SET = CLEAR = 1

7


NAND SR Latch

 

- Negative Pulse on SET input put the latch in a HIGH (SET) state


8

NAND SR Latch

 

- Negative Pulse on CLEAR input put the latch in a LOW (Clear or RESET) state.

NAND SR Latch

 



Set	Clear	Output
1	1	No change
0	1	Q = 1
1	0	Q = 0
0	0	Invalid*

*produces $Q = \bar{Q} = 1$



(b)

- Truth table for the NAND Set-Clear (Set-Reset or SR) Latch


NAND SR Latch

  

NAND SR Latch to deglitch a switch

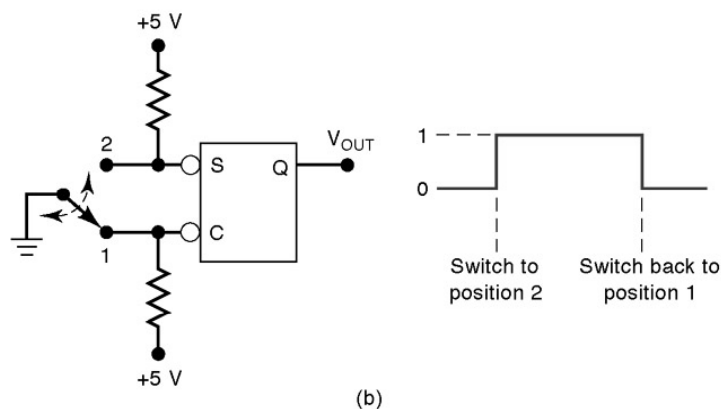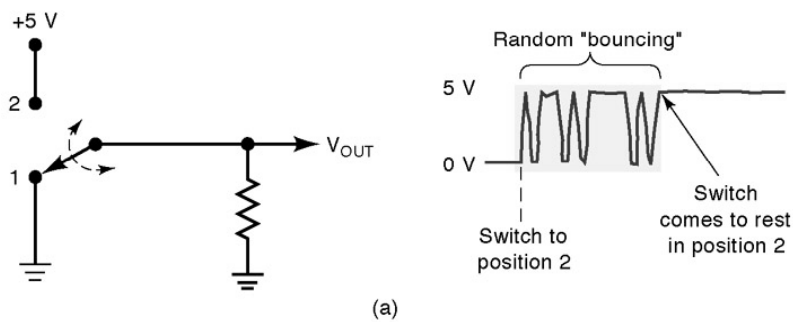


NOR SR Latch

 


Set	Clear	Output
0	0	No change
1	0	$Q = 1$
0	1	$Q = 0$
1	1	Invalid*

*produces $Q = \bar{Q} = 0$

(b)

 

(c)

 

13

Clocked Flip-Flop Circuits




- Digital systems can operate
 - **Asynchronously:** output can change state whenever inputs change
 - **Synchronously:** output only change state at clock transitions (edges)

14

Clocked Flip-Flop Circuits


■ Clock signal

   - Outputs change state at the edge (transition) of the input clock
- Positive-going transitions (**PGT**)
- Negative-going transitions (**NGT**)





Clocked S-R FF

 - On positive-going edge of a clock pulse





Inputs			Output
S	C	CLK	Q
0	0	1	Q ₀ (no change)
1	0	1	1
0	1	1	0
1	1	1	Ambiguous

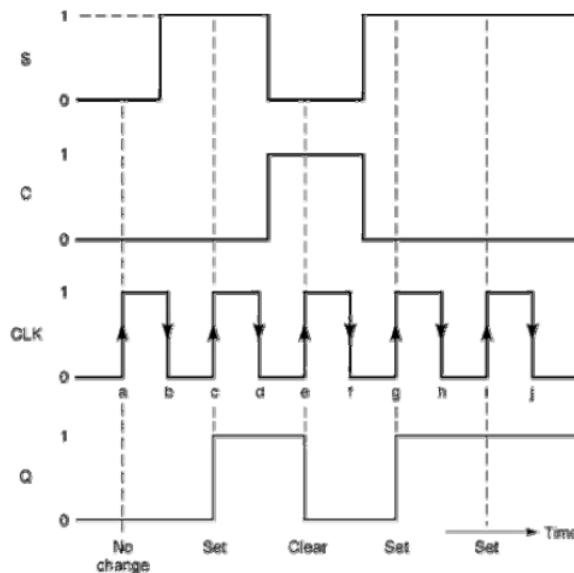 Q₀ is output level prior to ↑ of CLK.
↓ of CLK produces no change in Q.






Clocked J-K FF

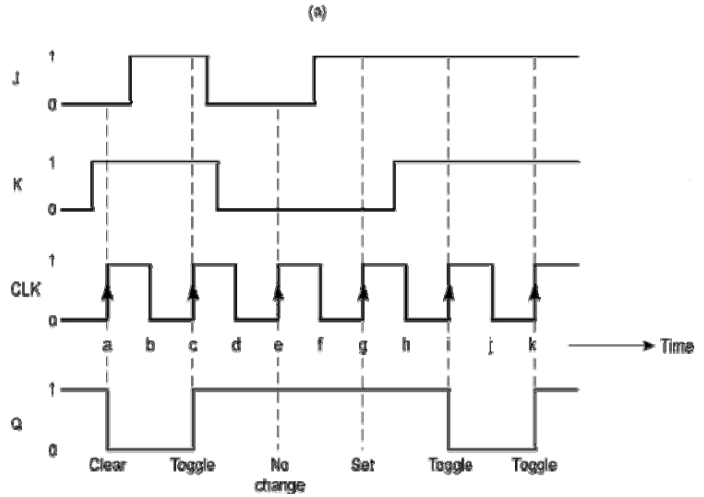 - J=K=1 condition does not result in an ambiguous output



Clocked D Flip-Flop

- It can be obtained from J-K Flip-Flop

   


Registers

- A register is a digital electronic device capable of storing several bits of data
 - Normally made from D-type flip-flops with asynchronous RESET inputs
 - Operates on the bits of the data word in parallel
 - Data on each data input is stored in the flip-flop on the rising edge of CLOCK
 - The data can be read from the Q outputs
 - The register can be cleared (zeroed) by asserting the CLEAR inputs


19

3-bit Parallel in/Parallel out

 



20

Shift Registers

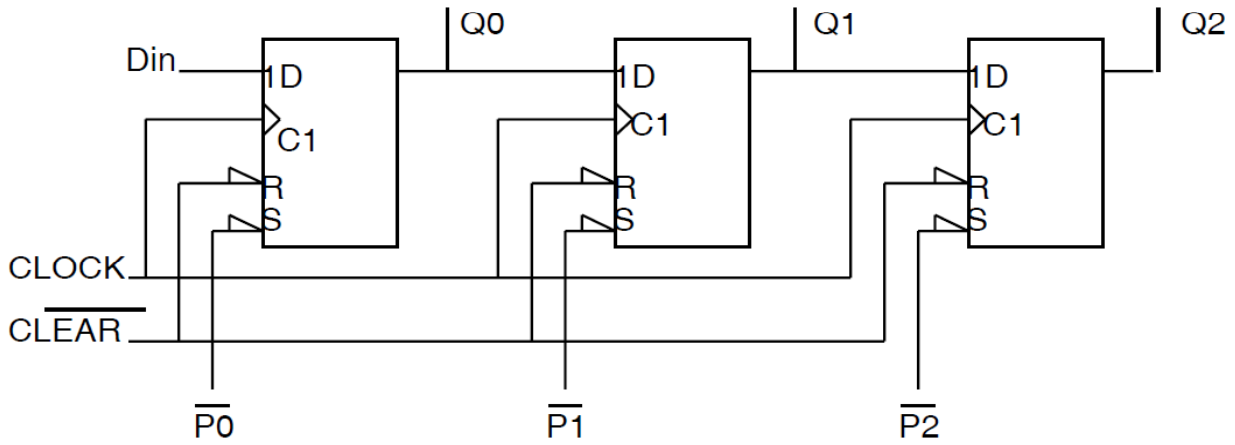



Divide by 2 Circuit

  - Consider a D-type flip-flop with Q connected to D



- The frequency of Q is half the frequency of CLOCK

Asynchronous Binary Counters

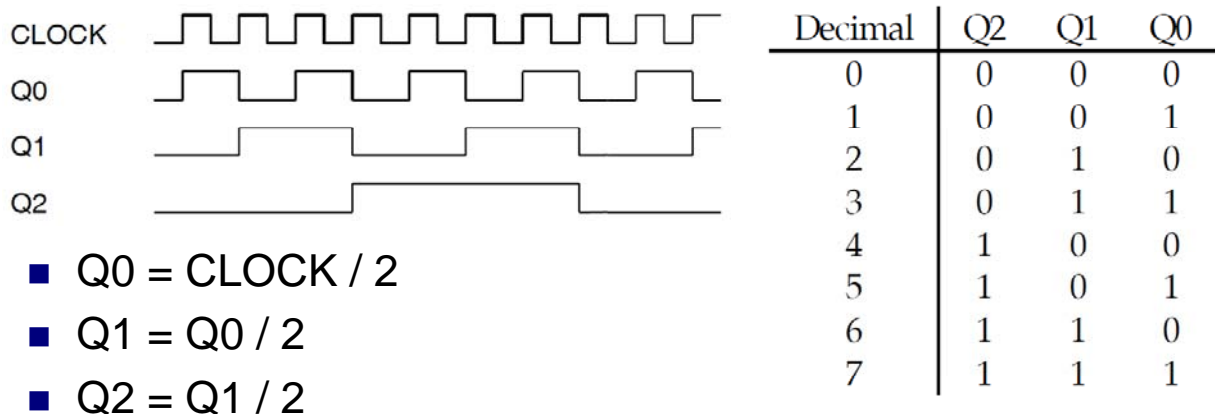 

23

Asynchronous Binary Counters

■ Limitations

- Consider the change from count 3 to count 4
 1. CLOCK goes from low to high
 2. Q0 goes from high to low
 3. Q1 goes from high to low
 4. Q2 goes from low to high
- The "CLOCK-TO-Q" delay of a typical flip-flop is about 30 ns
- Hence total time needed is about 90 ns.
- Hence max CLOCK frequency is = 11.1 MHz

24